

## Physics Laboratory Report

**Lab Number and Title:** Lab 217: RC Circuits

**Name:** Sundeep Singh

**Group Number:** 8

**Date of Experiment:** 04-01-2019

**Date of Report Submission:** 04-08-2019

**Course & section number:** Physics 121A-010    **Instructor's Name:** Kai Qian

**Partner's names:** Saga Elsekhely, Redhwan Rahi, Katherine Thai

---

### Introduction:

In Lab 205, the objective was to learn to observe and analyze the voltage across a capacitor  $V_c$  as a function of time  $t$  in a circuit containing a resistor and capacitor connected in series. The theories we had to know were the discharge of a capacitor and the charging of a capacitor.

### Experimental Procedure:

For Part I, we had to discharge a capacitor and for discharging a capacitor, when  $t$  is less than 0, the switch is in position A and the voltage on the capacitor,  $V_o$ , and since  $V_o = V_c$ , there is no current in the charging capacitor. When the switch is suddenly moved to position B, the capacitor discharges through the resistor  $R$ . When the switch was flipped we measure the voltage drop every 10 seconds. For part II, in the scenario when charging the capacitor, the switch is in position B rather than A and the voltage on the capacitor is 0. When the switch is moved to position A, the voltage  $V_o$  is applied to the RC circuit. Hence, the capacitor is being charged through the resistor  $R$ . Similar to part I, we measured the voltage every 10 seconds.

### Results:



Part A

Part I

$T_{exp}$ [s]	0	5	10	15	20	30	40	50	60
$V_{exp}$ [V]	4.398	3.702	3.147	2.659	2.288	1.684	1.259	0.934	0.694

MATLAB code outcome

Theoretical time constant ( $\tau$ ) [s]	33
Experimental time constant ( $\tau_{exp}$ ) [s]	33.7560
Percent error ( $error$ ) [%]	2.2908

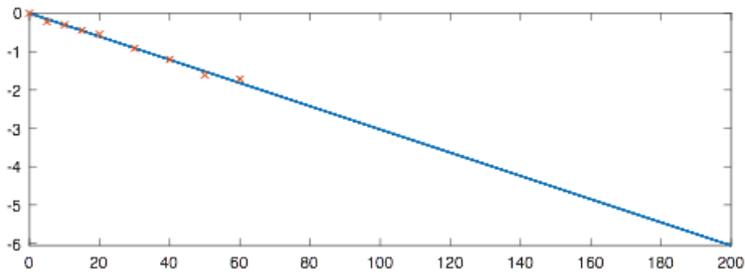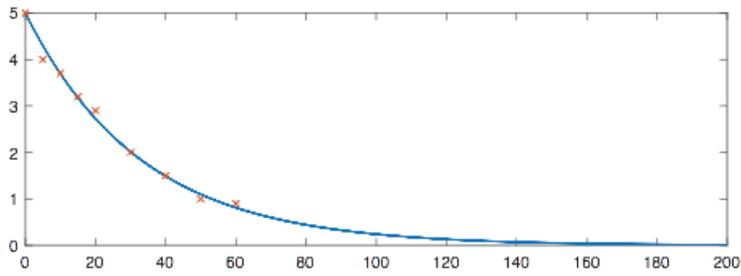



### Part II

Texp [s]	0	5	10	15	20	30	40	50	60	70
Vexp [V]	0.003	0.720	1.297	1.839	2.290	2.999	3.510	3.890	4.173	4.380

MATLAB code outcome

Theoretical time constant ( <b>tau</b> ) [s]	33
Experimental time constant ( <b>tauexp</b> ) [s]	33.0548
Percent error ( <b>error</b> ) [%]	0.1662

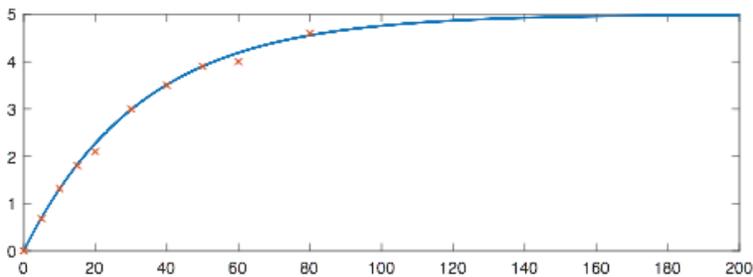

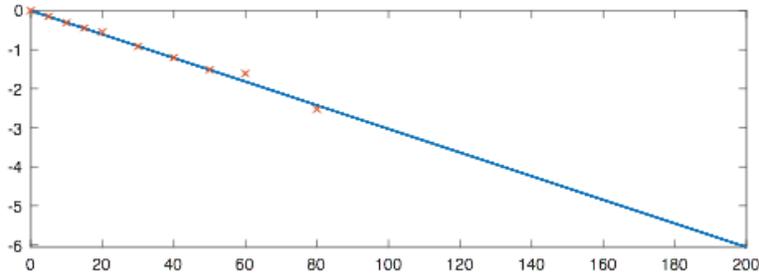

Part B:

	Voltage [V]	Time [s]	Time Changing [s]	Half-life [s]
Initial time (t0)	3.89850	(t0) = 0.12490	NA	NA
Half-life (t1)	1.94925	(t1) = 0.12800	(t1-t0) = 0.0031	tau1 = (t1-t0) = 0.0031
Two half-lives (t2)	0.98318	(t2) = 0.13110	(t2-t0) = 0.0062	tau2 = (t2-t0)/2 = 0.0031
Three half-lives (t3)	0.49502	(t3) = 0.13420	(t3-t0) = 0.0093	tau3 = (t3-t0)/3 = 0.0031
Averaged half-life [s]				(tau1+tau2+tau3)/3 = 0.0031
Experimental time constant [s]				(tau1+tau2+tau3)/(3*ln2) = 0.004472355
Theoretical time constant [s]				R*C = 0.0047
Percent Difference [%]				4.96372%

Measure the slopes and calculate relative time constants

Slope of Graph 1	-212.76
Time constant 1 [s]	0.0047
Slope of Graph 2	-212.75
Time constant 2 [s]	0.0047

$$\text{Slope} = -\left(\frac{1}{RC}\right)$$

Percent difference compare with theoretical time constant in Analysis 1

Time constant 1	0%
Time constant 2	0%

**Analysis (Results):**

Max: T = 0.12490 s      V = 3.89850 V

Half Life: T = 0.12800 s      V = 1.94925 V

Time-difference: 0.12800 - 0.12490 = 0.0033 s

Half-Life:  $\frac{0.12800 - 0.12490}{1} = 0.0033 \text{ s}$

¼ of max: T = 0.13110 s      V = 0.98318 V

Time-difference: 0.13110 - 0.12490 = 0.0062 s

Half-Life:  $\frac{0.13110 - 0.12490}{2} = 0.0033 \text{ s}$

⅓ of max: T = 0.13420 s      V = 0.49502 V

Time-difference:  $0.13420 - 0.12490 = 0.0093 \text{ s}$

Half-Life:  $\frac{0.13420 - 0.12490}{3} = 0.0033 \text{ s}$

Average half-life:  $\frac{0.0033 + 0.0033 + 0.0033}{3} = 0.0033 \text{ s}$

Experimental time constant:  $\frac{0.0033 + 0.0033 + 0.0033}{3 \cdot \ln(2)} = 0.004472355 \text{ s}$

Theoretical Time Constant:  $(10 \cdot 1000) \cdot (0.47 \cdot 10^{-6}) = 0.0047 \text{ s}$

% Difference:  $\frac{|0.0047 - 0.004472355|}{\frac{0.0047 + 0.004472355}{2}} * 100 = 4.96\%$

Time Constant 1:  $\frac{-1}{-212.76} = 0.0047 \text{ s}$

Time Constant 2:  $\frac{-1}{-212.75} = 0.0047 \text{ s}$

% Difference for time constant 1:  $\frac{|0.0047 - 0.0047|}{\frac{0.0047 + 0.0047}{2}} * 100 = 0.007\%$

% Difference for time constant 2:  $\frac{|0.0047 - 0.0047|}{\frac{0.0047 + 0.0047}{2}} * 100 = 0.007\%$

### **Conclusion:**

Overall, this lab further reinforced the topics we had learned in Physics lecture. For instance, we had learned about the concepts of discharging and charging a capacitor. Additionally, we learned that charging and discharging of the capacitor happens with an exponential ratio which is shown on the graphs.